

The exam has 100 pts. Closed book, no calculators. Write all answers and show all work inside your blue book. Read carefully.

Problem 1 (5 pts).

Convert the following to the specified number system.

- (a) ADC_{16} to Octal.
- (b) $0100\ 0101_2$ to Decimal.
- (c) 909_{10} to Binary.
- (d) 86_{10} to Hexadecimal.
- (e) 132_4 to Decimal.

Problem 2 (5 pts).

Perform the following computation, $13_{10} - 25_{10}$, in a two's complement binary number system. Verify that your answer is correct by converting your answer back to decimal.

Problem 3 (14 pts).

Consider the following boolean expression,

$$X = \overline{\overline{D} + B} + A(\overline{\overline{A} + BC}) + (D + \overline{B})\overline{C}B\overline{A}D$$

- (a) Write X in a sum-of-products form.
- (b) Convert X to a truth-table.
- (c) Use a Karnaugh-map to simplify X from its truth table.
- (d) Draw a logic diagram for the simplified expression. Label all inputs and outputs.

Problem 4 (8 pts).

- (a) Write the truth-table, corresponding boolean expressions, and a logic symbol for a 1:2 **demux**.
- (b) Draw the logic diagram of a 1:8 demux using your 1:2 demux symbols.
- (c) Draw the logic diagram of a 1:16 demux using your 1:8 demuxes symbols.

Problem 5 (14 pts). For each of the follow gates, write an equivalent boolean expression using only NOR expressions, and draw the corresponding logic diagram (using only NOR gates).

- (a) NOT
- (b) OR
- (c) AND

Problem 6 (20 pts).

In this problem, you will build a digital comparator that takes two N -bit binary numbers, A and B , and sets separate pins E , G , or L to high if $A = B$, $A > B$, or $A < B$, respectively.

- Write the truth-table for a *half-comparator* which takes as input two 1-bit binary numbers, A and B , and outputs E , G , and L .
- Determine boolean expressions of E and G . Express L in terms of E and G .
- A 1-bit *full-comparator* optionally takes as input the E and G results from another comparator (acting on more significant bits). Determine boolean expressions for the E , G , and L outputs of a 1-bit full-comparator in terms of A , B , E_{in} , and G_{in} .
- Draw a logic diagram for the 1-bit full-comparator. Draw a corresponding symbol to represent it.
- Draw a logic diagram for a 4-bit full-comparator, comparing $A_3A_2A_1A_0$ to $B_3B_2B_1B_0$ (left MSB), using 1-bit full comparators. Label all inputs and outputs. Do not leave input pins floating.

Problem 7 (4 pts).

Describe similarities and differences between the *SR-latch* and the *Gated D-Latch*.

Problem 8 (10 pts).

Consider the circuit shown in Figure 1, with a D-latch and Master-minion D Flip-Flop. Complete the timing for outputs Q_L and Q_F .

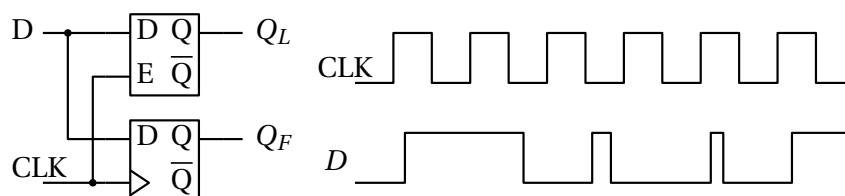


Figure 1: D-latch and MM D-FF circuit with corresponding input timing diagram.

Problem 9 (20 pts).

In this problem, you will build a synchronous “triggerable” Mod-4 binary **down** counter with positive edge-triggered D flip-flops. Specifically, from the $Q_1Q_0 = 11$ state the counter will only proceed to the next state when an external input T is high, otherwise it will remain in the 11 state. At all other states the input T has no effect on counting.

- Construct a state transition diagram for your counter.
- Convert your state transition diagram to a table, labeling current states, inputs, control variables, and next states. Determine values for your control variables to achieve the desired transitions.
- Determine simplified boolean expressions for your control variables.
- Draw a logic diagram of your circuit. Label the clock, T , and your state variables clearly.